

Total No. of Questions : 6

Total No. of Printed Pages : 6

158230017

EIS-179**B.E. (IInd Sem.) (CGPA) Civil Engg. Exam.-2016****BASIC ELECTRICAL & ELECTRONICS ENGG.****Paper - CE-203*****Time Allowed : Three Hours******Maximum Marks : 60*****Note :** Attempt all questions.

Question No. I is compulsory.

Q.I Choose the correct answer— 2 each

(i) The temperature coefficient of metal like copper, iron is—

2

- (a) Positive large
- (b) Negative large
- (c) Very small positive
- (d) Very small negative

(ii) The unit of power is—

- (a) Farad
- (b) Volt
- (c) Watts
- (d) Hertz

(2)

- (iii) The magnetic flux can be compared with —
- (a) Electro static flux (2)
 - (b) Electric current
 - (c) Magnetic current
 - (d) Magneto motive force
- (iv) The frequency of A.C. in India is—
- (a) 25 Hz
 - (b) 60 Hz
 - (c) 50Hz
 - (d) 100 Hz
- (v) Transformer core is laminated to reduce—
- (a) Copper loss (2)
 - (b) Windage loss
 - (c) Hysteresis loss
 - (d) Eddycurrent loss

Unit-I

Q.II (a) State and explain the following—

5

- (i) mmf & reluctance
- (ii) Statically and dynamically induced emf
- (iii) Ampere's circuitary law

(3)

- (b) In the circuit shown in figure-1 find current in various branch— 5

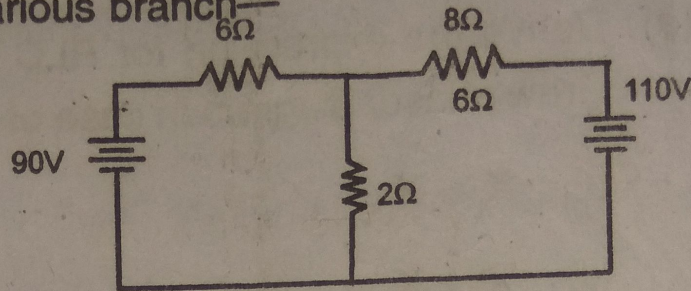


Figure-1

or

- (a) State and explain Kirchoff's current law and Kirchoff's voltage law. 5
- (b) (i) Compare the electric circuit with magnetic circuits 2
- (ii) State and explain thevenin theorem

Unit-II

- Q.III (a) Explain the following terms— 5

- (i) Form factor
- (ii) Peak factor
- (iii) Power factor
- (iv) Phase and phase difference

- (b) Draw 3 ϕ star connection and three phase delta connection and write down the equations for phase voltage, line voltage phase current and line current in both the cases. 5

(4)

or

- (a) Derive the expression for RLC series circuit. Draw phasor diagram in case of—

(i) $X_L > X_C$

(ii) $X_L < X_C$

Draw impedance triangle.

- (b) (i) What do you understand by three phase systems. Draw wave form of a three phase system.
- (ii) What are balanced load and unbalanced load.

Unit-III

- Q.IV (a) Explain working principle of a transformer. Derive the emf equation of transformer. What is transformation ratio. (5) 5

- (b) What are the various types of losses which occurs in a transformer. What is efficiency. 5 (3)

or

- (a) Draw the phasor diagram of transformer under no load and lagging load conditions.

(5)

- (b) Why we perform open circuit and short circuit test in a transformer. 5

Unit-IV

- Q.V (a) Explain the constructional features of a d.c. machine. 5

- (b) A 4-pole d.c. motor has a wave-wound armature with 594 conductors. The armature current is 40A and flux per pole is 7.5 mwb. Calculate H.P. of motor when running at 1400 rpm. 5

or

- (a) Draw the principle diagram of shunt wound. Series wound and compound generator. 5
- (b) Explain armature reaction. What are the effect of armature reaction and methods of compensating armature reaction. 5

Unit-V

- Q.VI (a) Draw PN junction diode. Explain depletion region and explain also the working of PN junction diode in forward biasing and reverse biasing mode. 5

(6)

- (b) Draw the block diagram of CRO and explain its various components. 5

2

or

- (a) Explain the following—

(i) Zener diode

(ii) Photo diode

(iii) BJT

- (b) Explain the characteristics and application of—

(i) UJT

(ii) Photo transistor